

科目：電子學乙 適用：電機所系統組

編號：432

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題  
共 2 頁  
第 / 頁

1. For the circuit shown in Figure 1, utilize the constant-voltage-drop model (0.5V) for each conducting diode, please draw the  $v_i$ - $v_o$  transfer characteristic plot. [10 分]

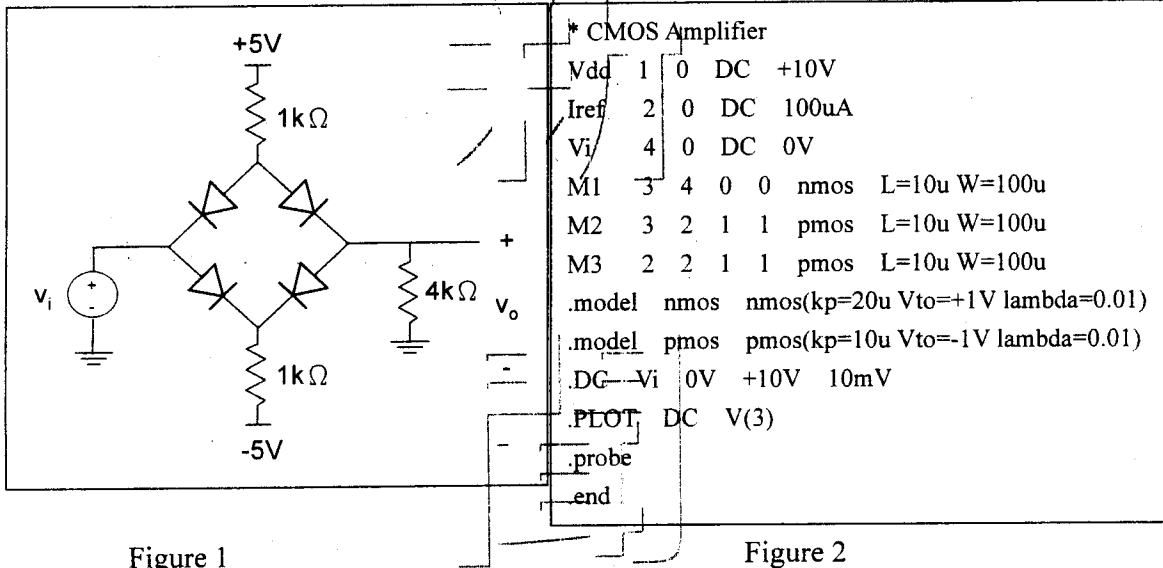


Figure 1

Figure 2

2. For the SPICE netlist shown in Figure 2. (a) Please redraw its circuit. (b) Find the small-signal voltage gain. (c) Also draw its  $v_i$ - $v_o$  transfer characteristic plot, please label the proper operation modes of transistors in the plot. ( $k_p = k'$ : process transconductance,  $V_{to}$ : zero-bias threshold voltage,  $\lambda = \lambda_A = V_A^{-1}$ : channel length modulation)

[(a) 5 分 (b) 7 分 (c) 8 分]

3. For the circuit shown in Figure 3, neglect base currents and use the exponential  $i_C$ - $v_{BE}$  relationship to show that

$$I_b = I_{ref} \sqrt{\frac{I_{S3} I_{S4}}{I_{S1} I_{S2}}}$$

( $I_S$  is the transistor's saturation current)

[10 分]

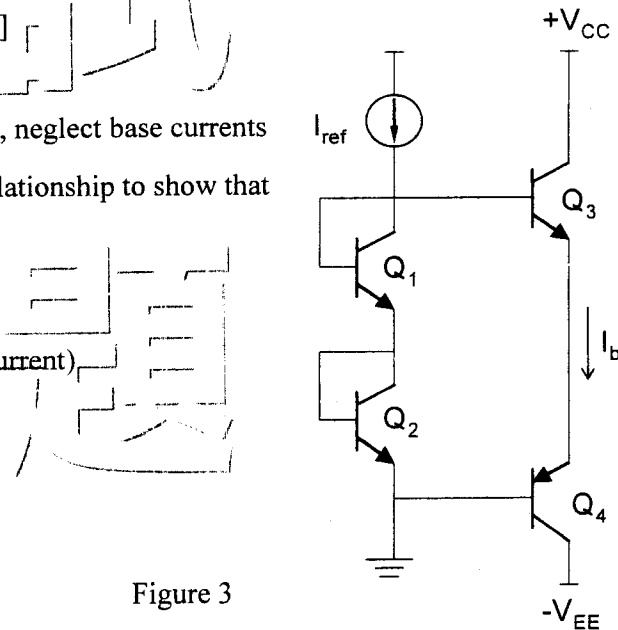




Figure 3

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題  
共 2 頁  
第 2 頁

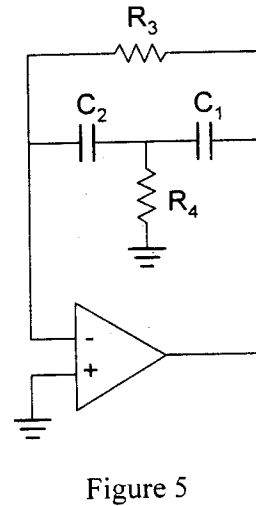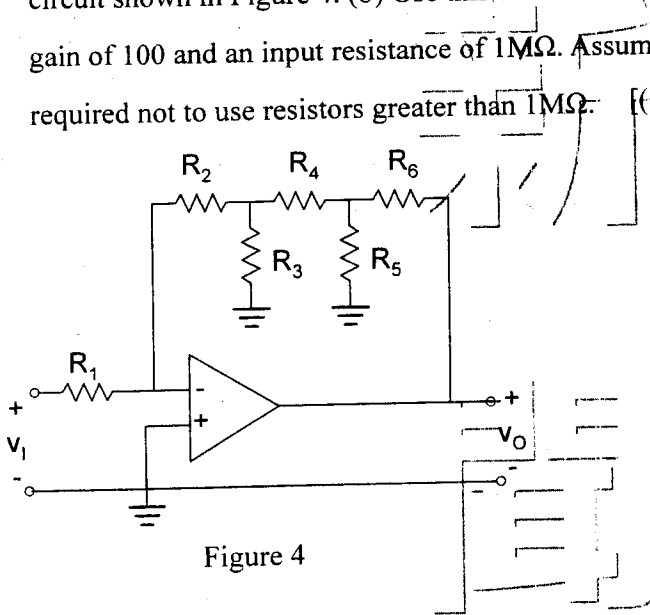
4. Assuming the op amp to be ideal, (a) please derive the close-loop gain  $v_o/v_i$  of the circuit shown in Figure 4. (b) Use this circuit to design an inverting amplifier with a gain of 100 and an input resistance of  $1M\Omega$ . Assume that for practical reasons it is required not to use resistors greater than  $1M\Omega$ . [(a) 10 分 (b) 10 分]



5. Assuming the op amp to be ideal, (a) please derive the open-circuit voltage transfer function of the RC network shown in Figure 5. (b) If  $R_1=R_2=R$  and  $C_1=C_2=C$ , and denote  $CR=\tau$ , please find the poles of the closed-loop amplifier. [(a) 10 分 (b) 10 分]

6. For the amplifier shown in Figure 6, uses transistors with  $\beta=100$ , please evaluate the following:

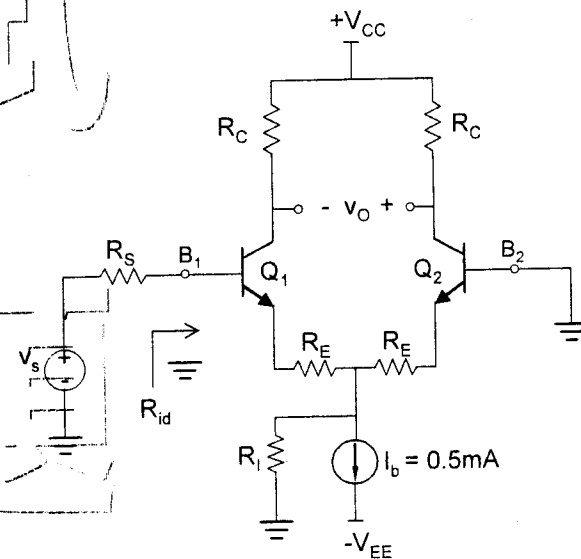- (a) The input differential resistance  $R_{id}$ .
  - (b) The overall voltage gain  $v_o/v_s$  (neglect the effect of  $r_o$ ).
  - (c) The worst-case common-mode gain if the two  $R_C$ s are accurate to within  $\pm 2\%$ .
  - (d) The CMRR, in dB. ( $\log 2 = 0.3$ )
- [(a) 5 分 (b) 5 分 (c) 5 分 (d) 5 分]



$(R_C=10k\Omega, R_S=10k\Omega, R_E=50\Omega, R_I=200k\Omega)$